


After successfully passing ECE3710, you created a brand new startup that builds inexpensive electronic gadgets out of old dismissed electronics.

Your new product is a signal generator that generates sine waves out of a square wave coming from an old microchip.


The square wave $x(t)$, shown in the block diagram below, has frequency $f = 300$ Hz and an amplitude of 2 V with 1 V DC offset. The square wave can be represented as:

$$x(t) = a_0 + a_1 \cos(1 \cdot \omega_0 t - \frac{\pi}{2}) + a_3 \cos(3 \cdot \omega_0 t - \frac{\pi}{2}) + a_5 \cos(5 \cdot \omega_0 t - \frac{\pi}{2}) + a_7 \cos(7 \cdot \omega_0 t - \frac{\pi}{2}) + \dots$$

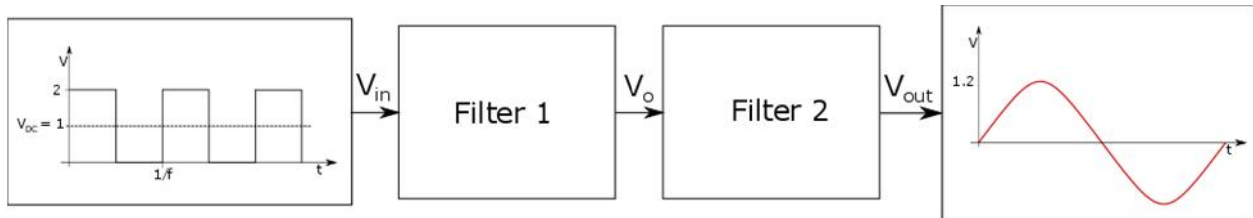With: $a_0 = 1$ and $a_n = \frac{4}{\pi n}$ $n = 1, 3, \dots$



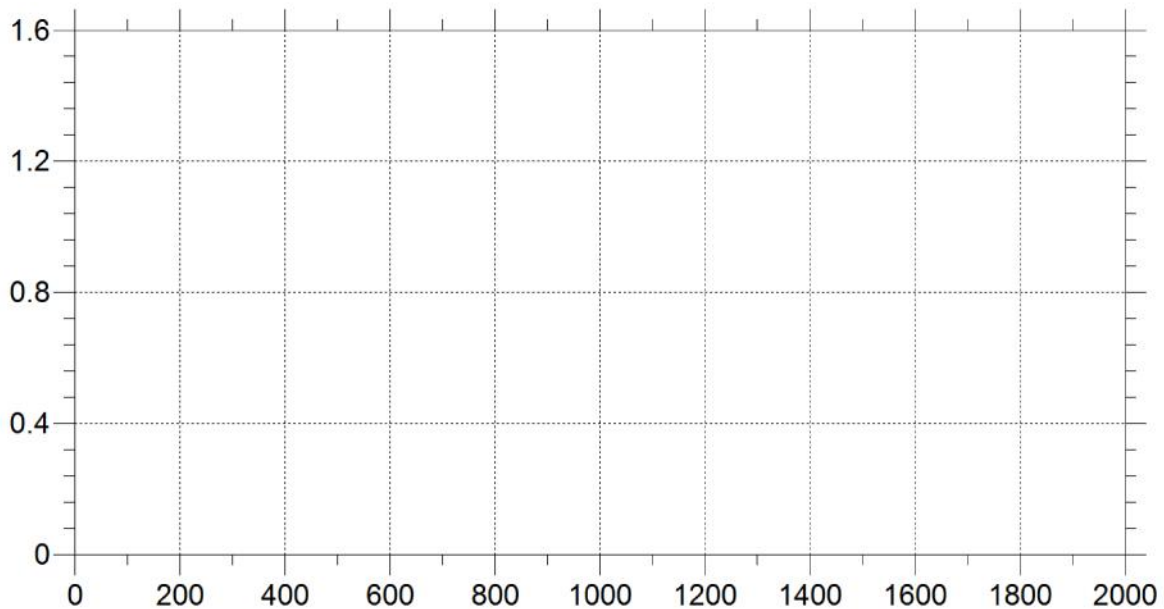A. Draw the frequency spectrum of the square wave $x(t)$:



B. To obtain a sine wave of frequency $f = 300$ Hz and 0 V DC offset, you need to properly filter the square wave signal.

Name the two 1st-order filters that you would use to obtain the desired output



Filter 1: _____

Filter 2: _____

For each filter, sketch the Bode plot (label the passband gains, the corner frequencies and the gains at the corner frequencies)

Filter 1:

Filter 2:

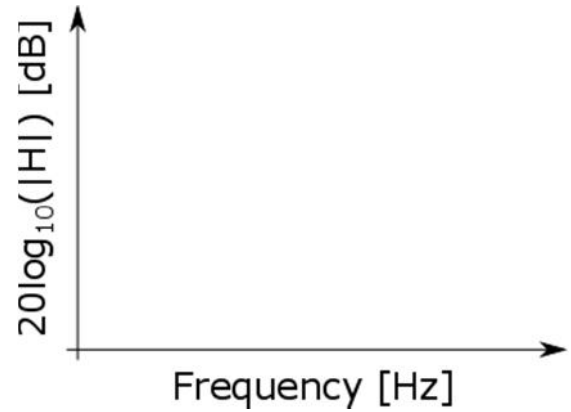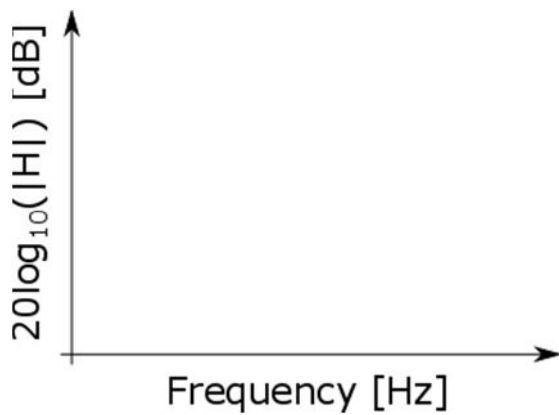


C. Draw the circuit schematic of the filters chosen in the previous section

Filter 1:



Filter 2:

 

D. Design the filters. For each filter, find the values of necessary R, C and/or L.

Show your work and don't forget the units.

Filter 1:

R: _____

C: _____

L: _____

Filter 2:

R: _____

C: _____

L: _____